

Chemistry 243 Winter Quarter 2017.  
R. Corn

Problem Set #3

Electrochemistry and Impedance Spectroscopy

1) Fick's Law Diffusion-limited Potential Step Measurements

a) For a diffusion-limited potential step, show that the Laplace transform for the concentration of the reactant  $C_O$  is given by:

$$C_O(x, s) = \frac{C_O^*}{s} - \frac{C_O^*}{s} \exp\left(-\sqrt{\frac{s}{D_O}} x\right)$$


Where  $C_O^*$  is the bulk concentration and  $D_O$  is the Diffusion Constant.

b) Please use the inverse Laplace transform to find  $C_O(x, t)$ , and plot  $C_O(x, t)$  vs.  $x$  for  $t = 1$  ms, 100 ms, and 1 sec for the case where  $C_O^* = 1$  mM and  $D_O = 5 \times 10^{-6}$  cm<sup>2</sup> s<sup>-1</sup>.

c) Please use Fick's first law in LaPlace space to get the Laplace transform of the current  $I(s)$ . Then use the inverse LaPlace Transform to find  $I(t)$ . This is called the Cottrell Equation.


EC Impedance Measurements.

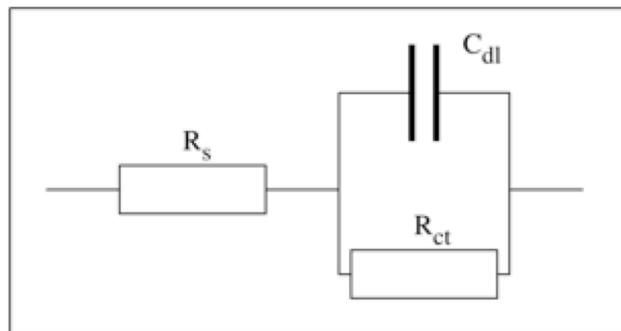2) Generate a Nyquist Impedance Plot and Bode Impedance plots (both magnitude and phase) for an angular frequency range of  $10^{-2}$  rad s<sup>-1</sup> to  $10^8$  rad s<sup>-1</sup> for a charge transfer system with no diffusion effects (Randles Cell):



Where  $R_s = 1000$  ohms,  $R_{ct} = 2000$  ohms, and  $C_{dl} = 2.0$   $\mu$ F.

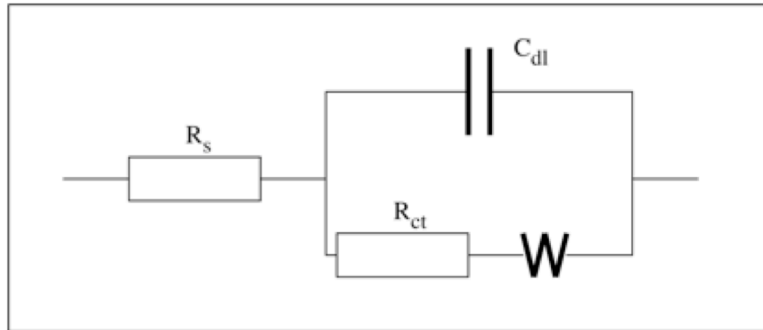3) Generate a Nyquist Impedance Plot and Bode Impedance plots (both magnitude and phase) in a frequency range of  $10^{-2}$  rad  $s^{-1}$  to  $10^8$  rad  $s^{-1}$  for a charge transfer system with diffusion effects (Randles-Ershler Circuit):



Where  $R_s = 1000$  ohms,  $R_{ct} = 2000$  ohms,  $C_{dl} = 2.0 \mu\text{F}$  and  $\sigma = 1000$  ohm  $\text{rad}^{1/2} \text{s}^{-1/2}$ .